

19.)  $R = 20 \Omega$     $\mathcal{E}_1 = \mathcal{E}_2 = \mathcal{E}$     $R_{b1} = R_{b2} = R_b$     $0,75 U_{kp} = U_{ks}$

a.)  $R_b = ?$

b.)  $\frac{P_{Rs}}{P_{Rp}} = ?$


Kirchhoff I.  $\sum I_i = 0$

Kirchhoff II.  $\sum U_i = 0$

$$I = \frac{U}{R}$$

$$P = \frac{U^2}{R}$$

a.)

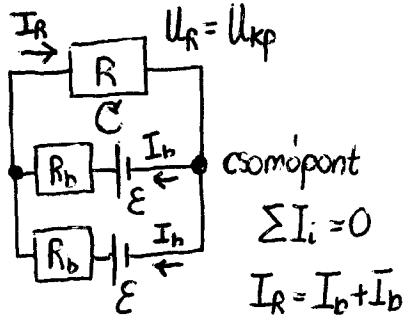

$\sum I_i = 0$

$I_R = I_b + I_b$

(1)  $I_R = 2I_b$

hurok:  $\sum U_i = 0$

$$\mathcal{E} - I_b R_b - I_R R = 0$$

$\underbrace{\hspace{2cm}}_{U_{kp}}$


$$I_b = \frac{\mathcal{E} - U_{kp}}{R_b}$$

(1) -be írva:

$$\frac{U_{kp}}{R} = \frac{2(\mathcal{E} - U_{kp})}{R_b}$$

$$R_b U_{kp} = 2\mathcal{E}R - 2U_{kp}R$$
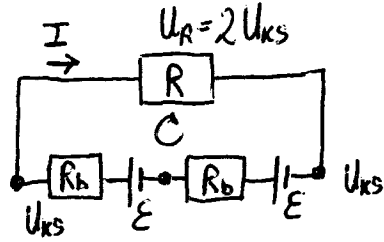
$$U_{kp} = \frac{2\mathcal{E}R}{R_b + 2R} \rightarrow$$



$$I = \frac{2U_{ks}}{R}$$

hurok:  $\sum U_i = 0$

$$\mathcal{E} - IR_b + \mathcal{E} - IR_b - IR = 0$$

$$2\mathcal{E} - 4 \frac{U_{ks}}{R} R_b = 2U_{ks}$$

$$2\mathcal{E} = U_{ks} \left( 2 + 4 \frac{R_b}{R} \right)$$

$$\frac{\mathcal{E}}{1 + 2 \frac{R_b}{R}} = U_{ks}$$

$$0,75 U_{kp} = U_{ks}$$

$$\frac{1,5\mathcal{E}R}{R_b + 2R} = \frac{\mathcal{E}}{1 + 2 \frac{R_b}{R}}$$

$$\Downarrow$$

$$\underline{\underline{R_b}}$$

b.)

$$\frac{P_{Rs}}{P_{Rp}} = \frac{\frac{4U_{ks}^2}{R}}{\frac{U_{kp}^2}{R}} = 4 \left( \frac{U_{ks}}{U_{kp}} \right)^2 = \dots$$